

What Is Electricity?

Electricity flows in the path of least resistance

From positive terminal on battery to negative*

From 5V out from the Arduino to ground

Voltage (volts) = flow

Voltage flows from a power supply into a device

Current (amps) = suck

Current is pulled from the power supply by the device

Resistance (ohms) = restriction

Resistance changes the amount of voltage

**Voltage from your supply should never be
more than your device can handle**

**USB sends out 5 volts
Your Arduino runs on 5 volts*
Happy Arduino!**

**The wall outlet sends out 120 volts
Arduino = smoke and sadness**

**Less voltage is sometimes ok (ex: it will make a motor turn slower)
Too much will damage your device but not your supply**

Voltage (volts) = flow

Voltage flows from a power supply into a device

Current (amps) = suck

Current is pulled from the power supply by the device

Resistance (ohms) = restriction

Resistance changes the amount of voltage

**Current needs of your device should
never be more than your supply can provide**

**Your Arduino pulls a max of ~500mA
USB is able to provide ~500mA
Happy USB!**

**A big motor attached to your Arduino pulls 2A
Sad Arduino and sad USB!**

**More current capacity from your supply is fine
Too little available current will damage your supply**

Voltage (volts) = flow

Voltage flows from a power supply into a device

Current (amps) = suck

Current is pulled from the power supply by the device

Resistance (ohms) = restriction

Resistance changes the amount of voltage

Analog sensors are (mostly) all resistive

Made of materials that change resistance under different conditions

Ex: light sensor lets more electricity through the more light there is

The analog pins measure the voltage, which gives us a reading!

**Sending 5V directly back into ground
is bad because it creates infinite current!**

(aka a short circuit)

This creates heat, smoke, and other bad things

Direct current (DC)

Continuous current at the same level

What nearly all consumer electronics run on

Alternating current (AC)

**Sinewave where current swings pos/neg
(Rate of 50Hz or 60Hz)**

**What comes out of your wall socket
And runs things like fridges and blenders**

Electricity = ~~Flow~~ Dangerous

(or, at least, it can be)

Never touch two wires together

Avoid wiring a circuit with your Arduino plugged in

Heatshrink or electrical tape!

Avoid anything that plugs into the wall

Voltage Divider

Review: we don't want all current flowing back into GND

The electricity needs to go somewhere

A “voltage divider” circuit lets us read other analog sensors

5V out from Arduino

Resistive sensor
(like a light sensor)

both connected here >>


Second resistor
(we need to calculate this value)

GND

Reading to analog pin



The diagram illustrates a voltage divider circuit. A vertical line represents the main power path. At the top, a horizontal line connects to the text '5V out from Arduino'. Below this, a blue rectangular block represents the 'Resistive sensor (like a light sensor)'. Further down, another blue rectangular block represents the 'Second resistor (we need to calculate this value)'. At the bottom, a horizontal line connects to the text 'GND'. A horizontal line branches off from the vertical line between the two resistors, pointing to the text 'Reading to analog pin'. A label 'both connected here >>' points to this junction.

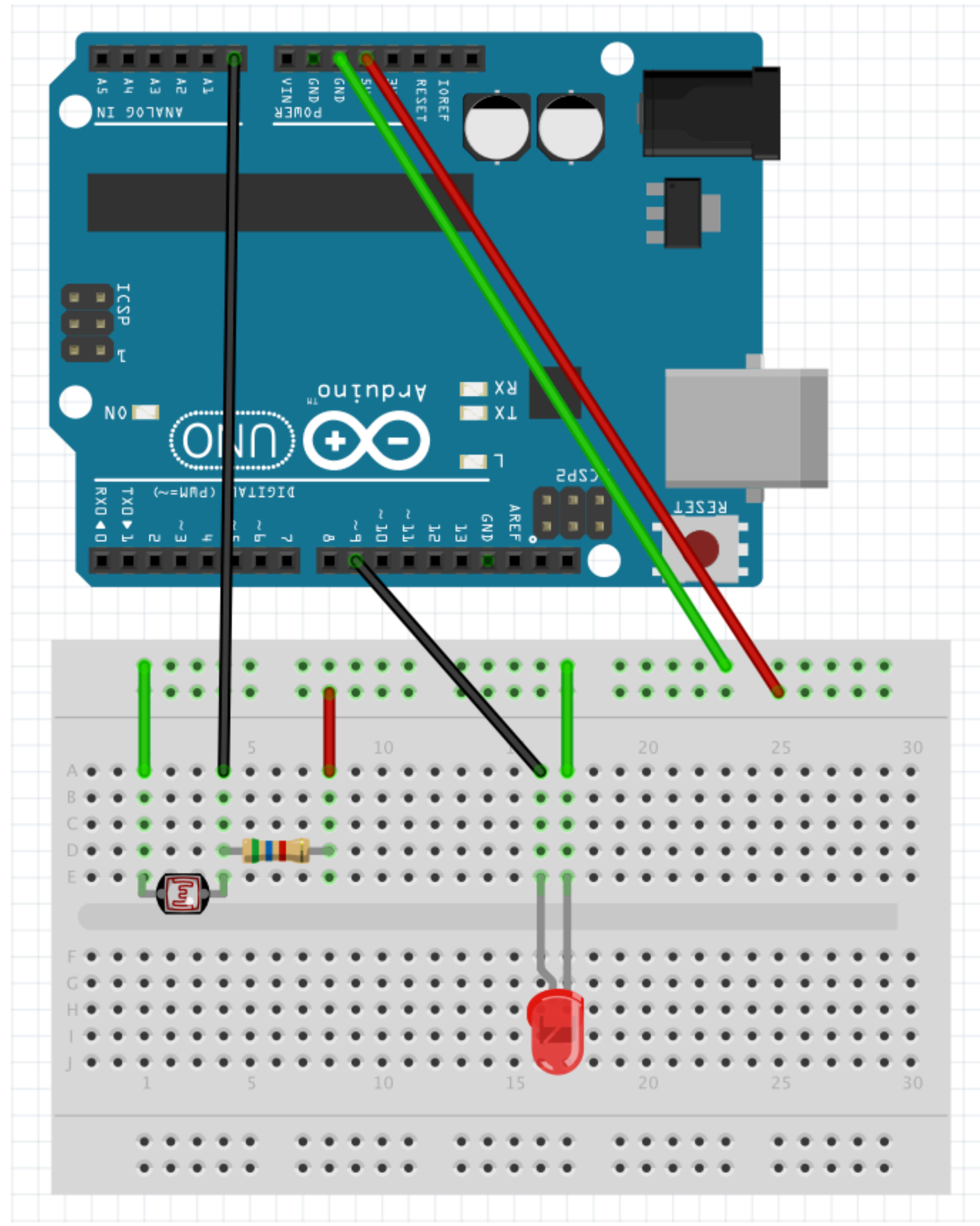

Steps

- 1. Measure the resistance of your sensor under two extremes**
- 2. Add the values and divide by two - this is your second resistor**
- 3. To find the voltages that will result:**
Ratio = Resistor value / (Sensor resistance + resistor value)
Resulting voltage = input voltage * ratio

Try measuring light and dark resistance of your LDR!

Find second resistor:

Light = 1 kΩ

Dark = 10 kΩ

2nd resistor = $(1k + 10k) / 2 = 5.5 kΩ$

Find voltages that will result:

Ratio = Resistor value / (Sensor resistance + resistor value)

Light ratio = $5.6 / (1+5.6) = 0.15$

Dark ratio = $5.6 / (10+5.6) = 0.67$

Light voltage = $5V \text{ from Arduino} * 0.15 = 0.75VDC$

Dark voltage = $5V \text{ from Arduino} * 0.67 = 3.35VDC$